
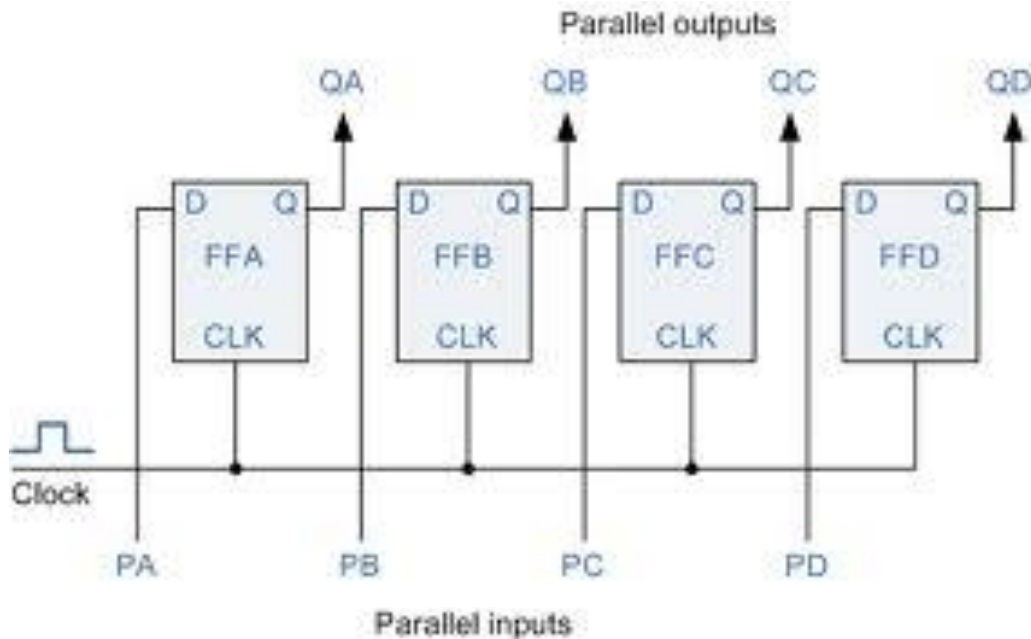


1. Registers

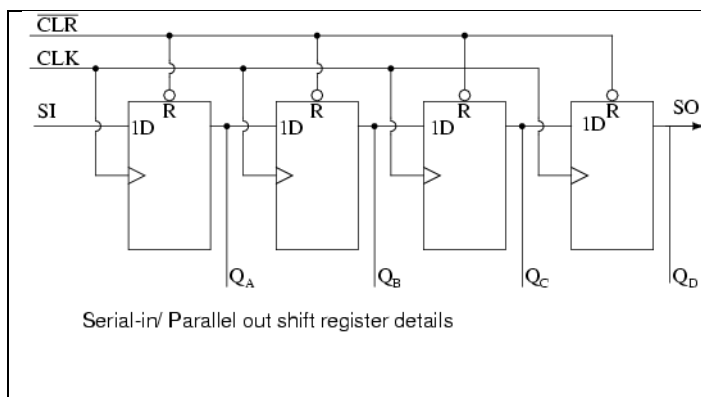
- a. Set of flip-flops used to store n bits of information
 - i. Common clock used for each flip flop in the register
- b. Parallel register – set of 1-bit memories that can be read or written simultaneously
 - i. Tend to use D flip flops, but can use others with some extra logic



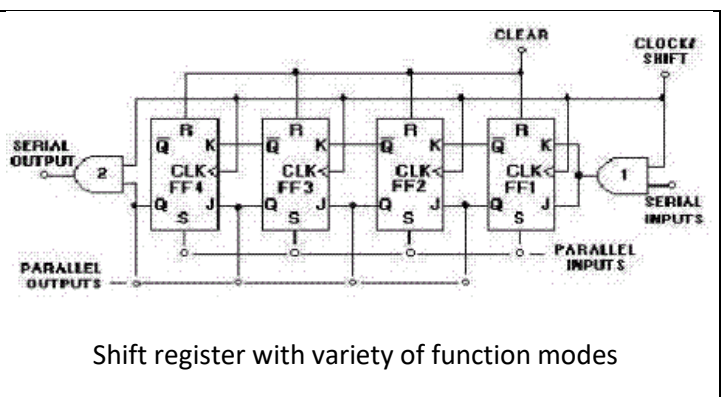- c. Shift register – register that accepts and transfers data serially
 - i. Takes previous values and shifts them over in register
 1. Equal to a queue – first in, first out or FIFO
 2. 4-bit example: push values into left side, values removed from right side
 - a. xxxx (to start)
 - b. 1xxx (input 1)
 - c. 01xx (input 0)
 - d. 001x (input 0)
 - e. 1001 (input 1)
 - f. 0100 (input 0)
 - ii. Interface with serial I/O devices, delay signals, do logical bit shifts in ALU
 - iii. Main idea – take previous FF value and pipe into current FF




Serial-in/ Parallel out shift register details



Shift register with variety of function modes

2. Counter

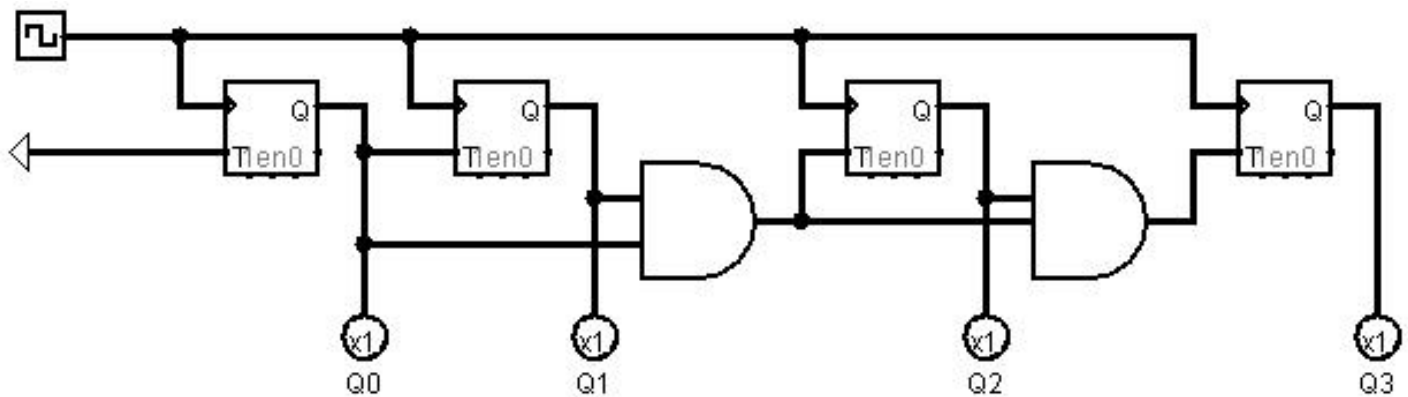
- a. Register whose value is easily incremented by 1
- b. Eventually “saturates” and reaches maximum value
 - i. When this happens, up to designer to decide what happens
 - ii. Can roll over, stay at value, start decrementing...
- c. Ripple (asynchronous) counters
 - i. Each FF waits for the previous FF before changing the signal
 - ii. Called asynchronous because some FFs in sequence don’t use the main clock
 1. Instead, those FFs use other FF outputs as their clock input
- d. Synchronous counter
 - i. Counter that has all FFs change at the same time based on main clock
 1. Hence *synchronous*, all dependent on main clock
 - ii. Far faster than a ripple counter
 - iii. How example below counts
 1. Start with all 0s
 2. When first flip flop (Q0) turns to 1, it’s toggled back to 0 on next cycle
 3. Next flip flop (Q1) in sequence turns 1 due to Q0 = 1
 4. When both of those flip flops turn to 1, because of the AND gate, third flip flop (Q2) turns to 1 as well
 5. Repeat for Q3 and further
 - iv. Below: synchronous implementation using T flip flops



3. Finite state machines (FSMs)

- a. Already seen these, actually
 - i. The state transition diagram that we drew for a S-R latch/flip-flop was an FSM
 - ii. Operation behind any latch or flip flop can be described by an FSM
- b. Definition
 - i. A circuit whose behavior can be modeled using the concept of “state” and the transitions between those states

4. FSM general format

 

- a. Moore model FSMs have outputs only dependent on the current state
 - i. Ripple counters, shift registers
- b. Mealy model FSMs have outputs dependent on the state and input
 - i. This is the dashed line in the diagram
 - ii. If input isn't clocked, output may change at any time in a clock cycle

5. FSM basic design steps

- a. Four step process, from word description to circuit
 - i. Turn a word description into a state diagram
 - 1. Seen this before
 - ii. Turn the state diagram into a transition table
 - 1. Also have seen this before
 - iii. Use transition table to make K-maps to simplify circuit
 - 1. Did K-maps previously, will use them again here
 - iv. Implement simplified circuit