
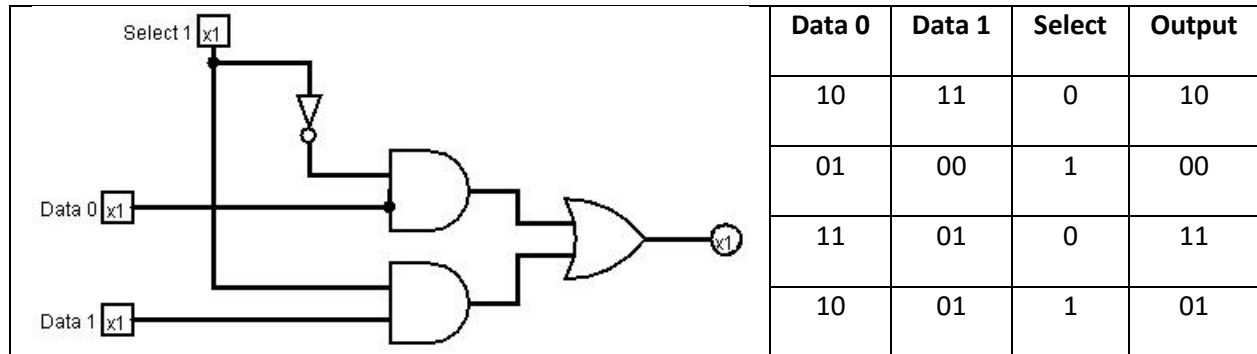


1. More on MUXes

 - a. Truth table for simple 2 data bit 2 to 1 MUX
  - i. Naming of MUX: (# of inputs) to (1 output) MUX
  - ii. Two inputs below, hence 2 to 1 MUX
- b. Idealized picture below




- c. Can use MUXes to implement functions
  - i. Hook up constant 0s or 1s to each input
  - ii. MUX takes in input bits and outputs corresponding constant for that input
  - iii. Example below: implement an AND gate using a 4 to 1 MUX
    1. Naming: 4 inputs to 1 output MUX




## 2. Decoders

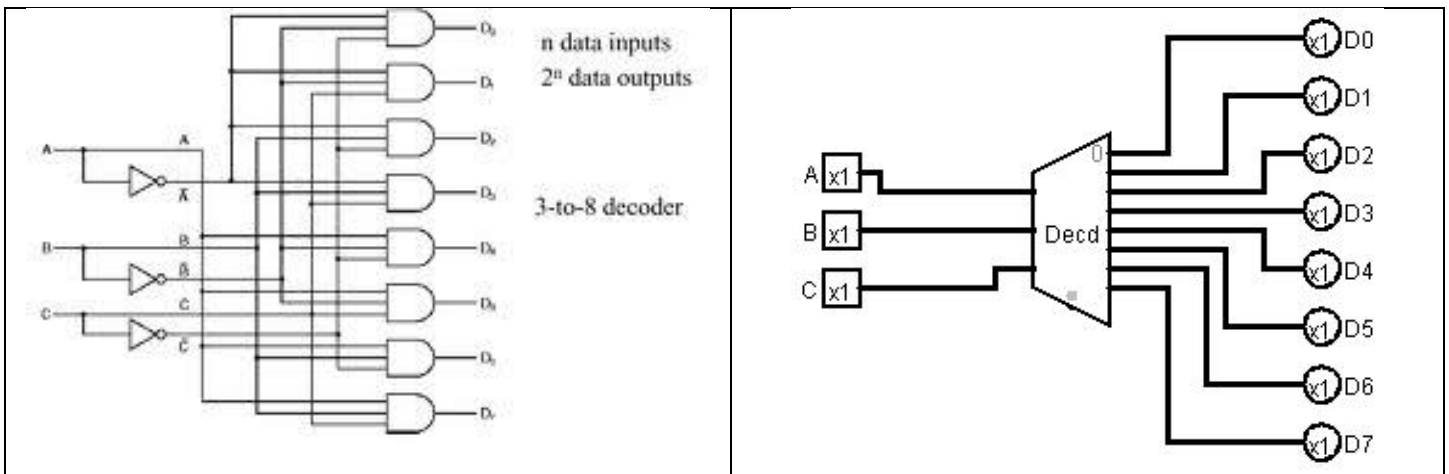- a. Decoders convert binary information from  $n$  input lines to a maximum of  $2^n$  unique output lines
  - i. Naming: (# of inputs) to (# of outputs) decoder
- b. One-hot encoded – only one output is asserted at a time
  - i. Used in memory circuits
    1. Give an encoded address, need to select a memory location
    2. Use a  $n$  to  $2^n$  decoder to convert the selected address on the bus to the correct row
  - ii. Can also use to implement regular Boolean functions
    1. Similar to a MUX function implementation
- c. Additional input attached to all AND gates can be used in two ways
  - i. If you use data, we turn the decoder into a *demultiplexer* (demux)
    1. Guides the input data into a specific output
  - ii. If we treat the line as an enable, we can turn the decoder on and off




## 3. Adder

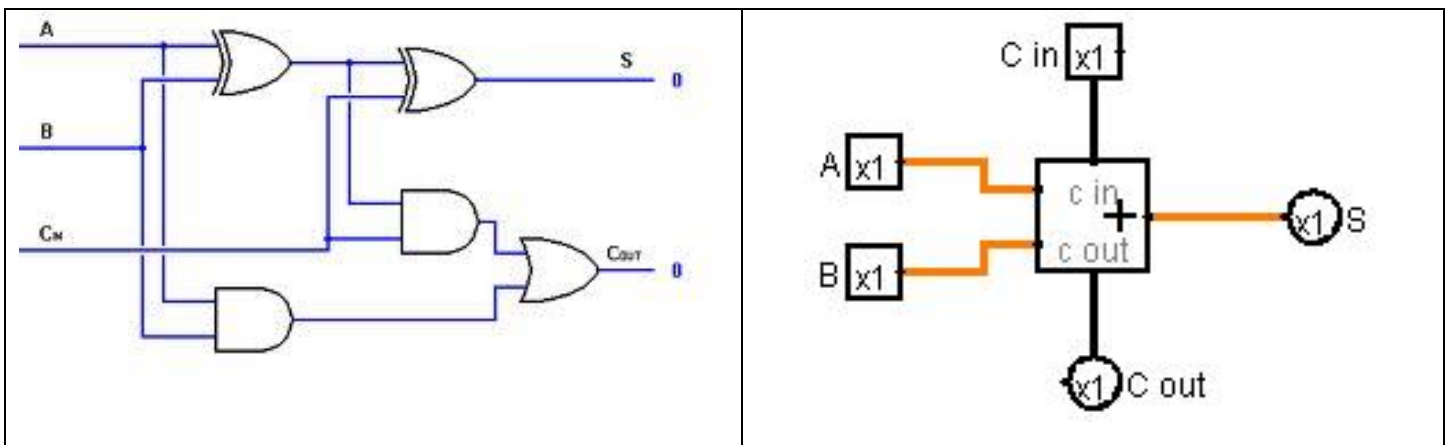- a. Digital circuit that adds two numbers
- b. *Half adder* – adds two single binary digits,  $A$  and  $B$ 
  - i. Two outputs, the sum  $S$  and carry  $C$
- c. *Full adder* – add binary numbers, account for carry in and carry out
  - i. Longest (worst-case) path ( $A$  to  $C_{out}$ ) goes through three gates
  - ii. Involved in determining clock speed




d. Types of multiple-bit adders

 - i. *Ripple-carry* – adder made up of a bunch of full adders hooked up in sequence
  1. Use the  $C_{out}$  of the previous bit being added as its  $C_{in}$
  2. Causes a delay as you need to wait for the carry signal to propagate through



4. Carry-lookahead adders (CLA)

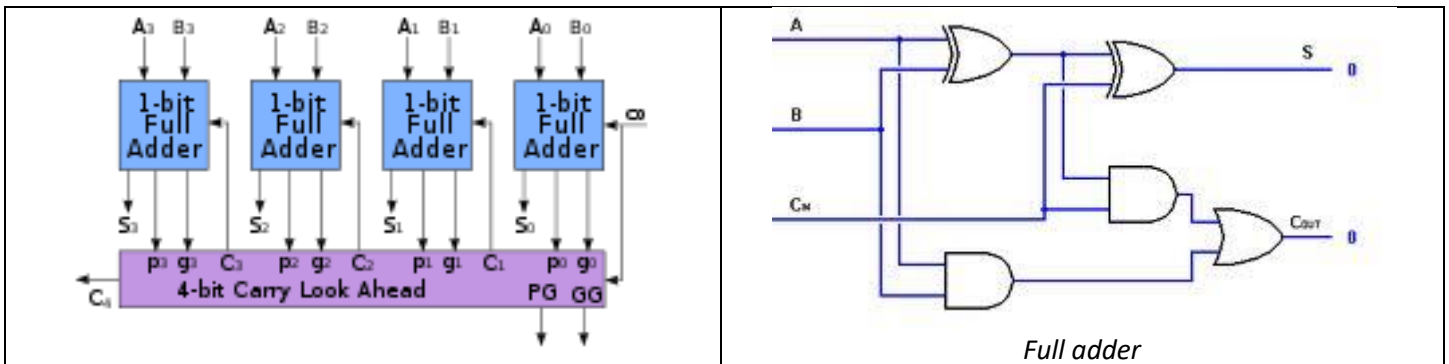

- a. Want to provide all carry bits for an adder at the same time
  - i. Don't want to have to wait for them to ripple through
- b. Generate two signals for each bit position
  - i. *Generate*, or  $g$ 
    1. Addition will always carry, doesn't matter if there's an input carry or not
    2.  $G(A, B) = A * B$
  - ii. *Propagate*, or  $p$ 
    1. Addition will carry whenever there is an input carry
    2.  $P(A, B) = A \oplus B$
- c.  $C_{i+1} = G_i + P_i C_i$ , where  $C$  is the carry
  - i.  $G_i = A_i B_i$ ,  $P_i = A_i \oplus B_i$
  - ii. Can expand this out
    1.  $C_1 = G_0 + P_0 * C_0$
    2.  $C_2 = G_1 + P_1 * C_1 = G_1 + P_1 * (G_0 + P_0 * C_0) = G_1 + P_1 * G_0 + P_1 * P_0 * C_0$
    3.  $C_3 = G_2 + P_2 * C_2 = G_2 + P_2 * (G_1 + P_1 * C_1) = G_2 + P_2 * (G_1 + P_1 * (G_0 + P_0 * C_0))$   
 $= G_2 + (P_2 * G_1) + (P_2 * P_1 * G_0) + (P_2 * P_1 * P_0 * C_0)$
    4.  $C_4 = G_3 + P_3 * C_3 = G_3 + P_3 * G_2 + (P_3 * P_2 * G_1) + (P_3 * P_2 * P_1 * G_0) + (P_3 * P_2 * P_1 * P_0 * C_0)$
  - iii.  $C_0$  is the only carry that must be known for all these calculations