
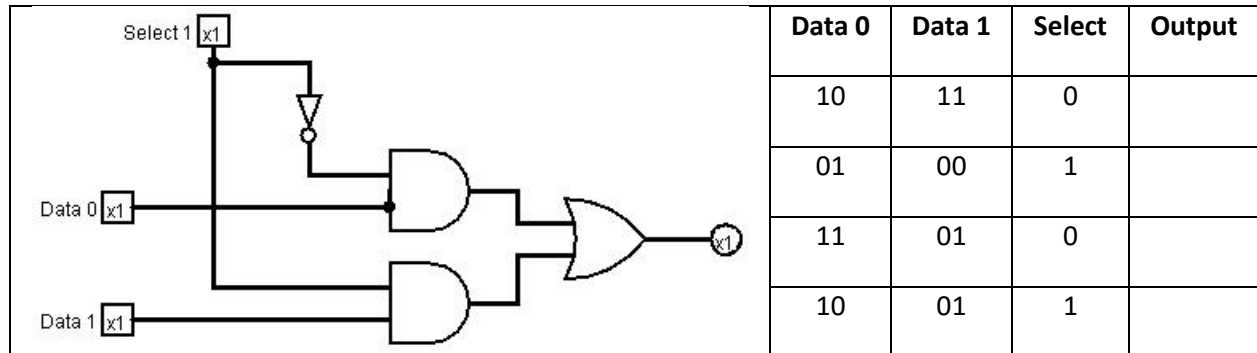


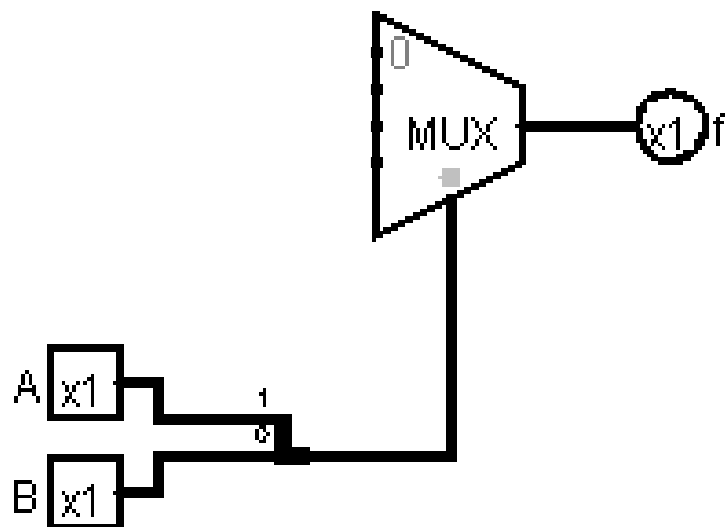1. More on MUXes
 - a. Truth table for simple 2-bit 2 to 1 MUX
 - b. Idealized picture below




- c. Can use MUXes to implement functions

- i. Example below: implement an AND gate using a 2 to 1 MUX




2. Decoders

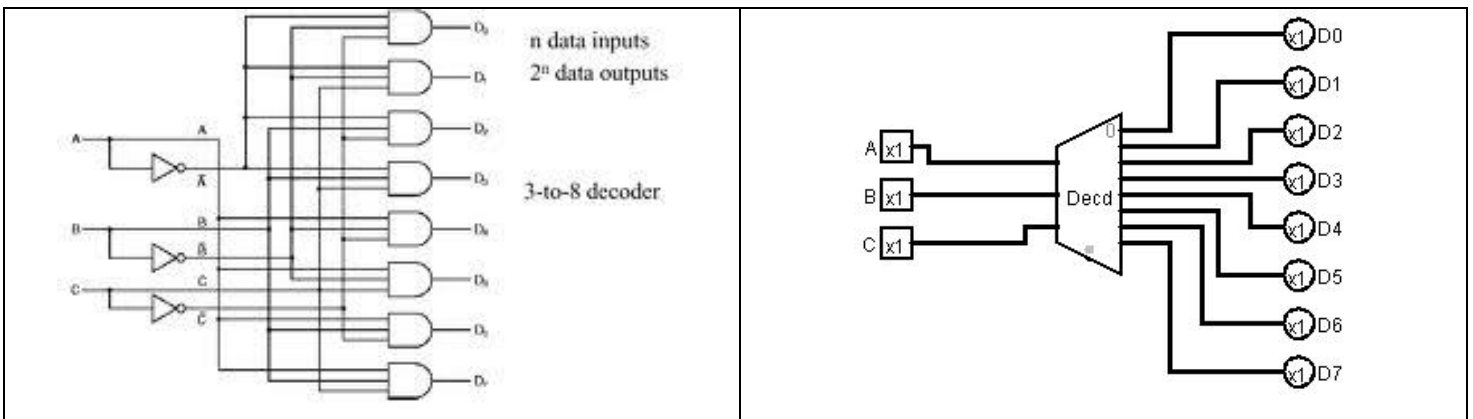- a. One-hot encoded
- b. Additional input attached to all AND gates can be used in two ways




3. Adder


- a. *Half adder*
- b. *Full adder*

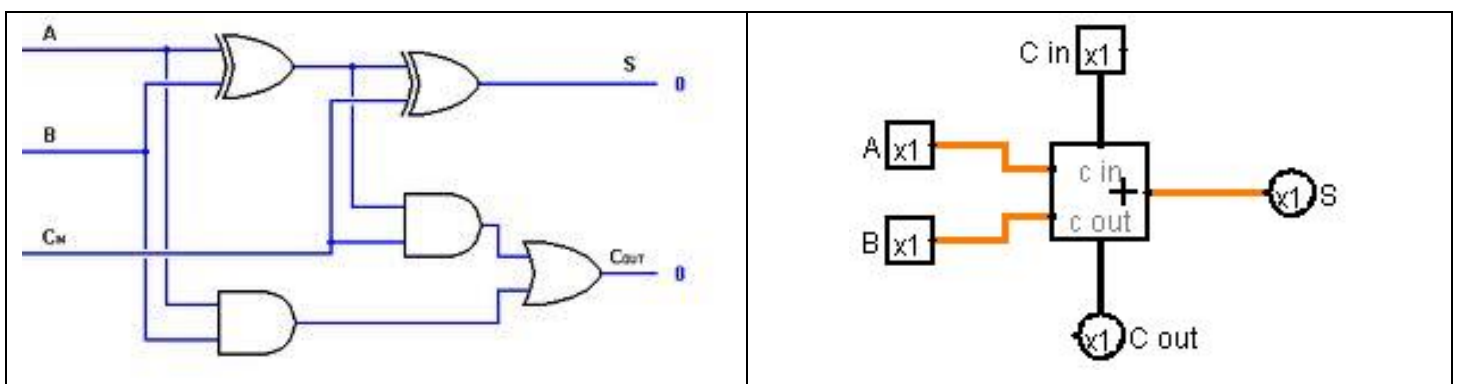

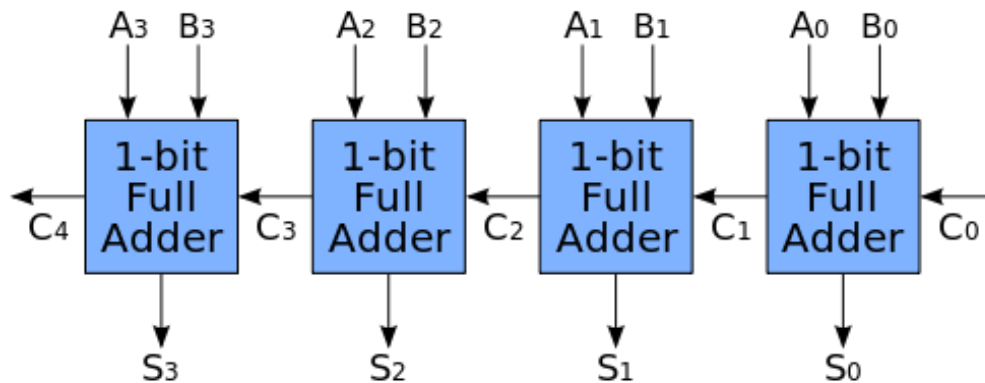- c. Types of multiple-bit adders
 - i. *Ripple-carry*



4. Carry-lookahead adders (CLA)

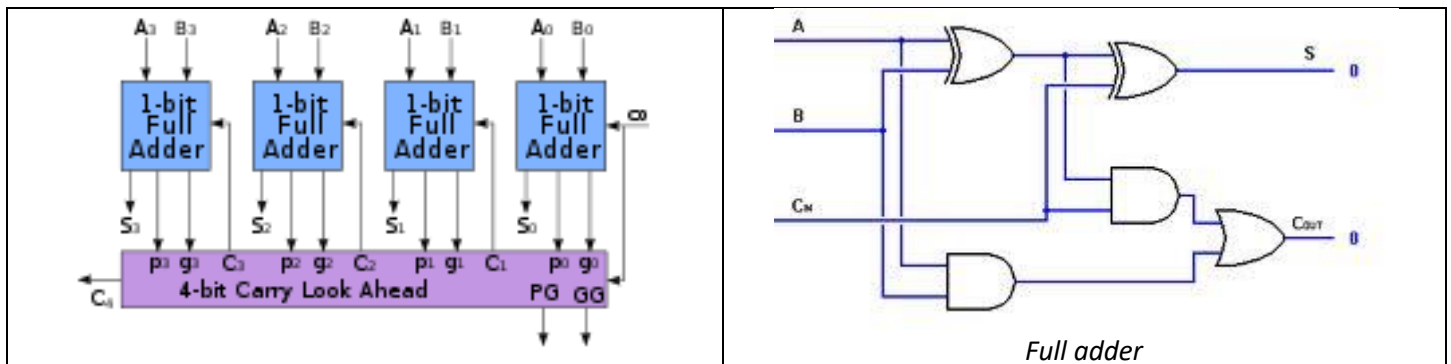

- a. Want to provide all carry bits for an adder at the same time

- b. Generate two signals for each bit position
 - i. *Generate*, or *g*

- ii. *Propagate*, or *p*

c. $C_{i+1} =$

i. $G_i =$

ii. $P_i =$

iii. Can expand this out

1. $C_1 =$


2. $C_2 =$

3. $C_3 =$

4. $C_4 =$

d. Process

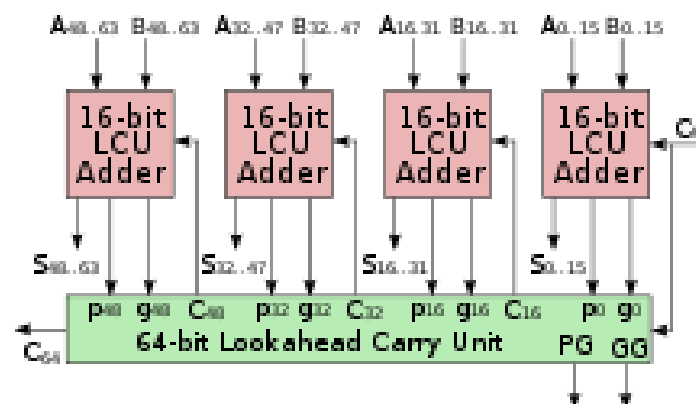e. Can expand this 4-bit adder to further levels



5. Subtractors

a. Circuit below

