
 



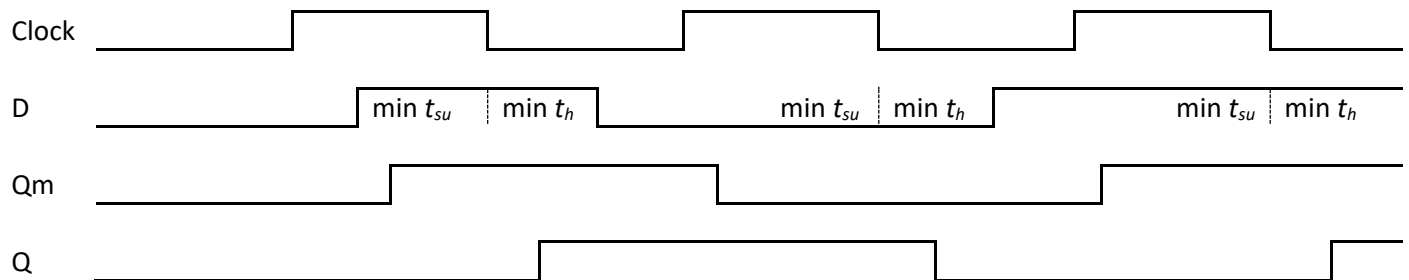
1. Falling edge-triggered master-slave D flip-flop



a. Timing diagram



2. Rising-edge triggered D flip-flop

  

3. Flip flop timing

- a. Two main times to consider for flip flops
  - i. Setup time

- ii. Flip flop propagation delay

- iii. Hold time – not important


- b. Keeping track of times in larger circuit diagrams
  - i. Inputs start at time 0

- ii. Flip flops start at their propagation delay

- iii. Calculating delays for each gate


c. Example

 - i. DFF setup delay = 4 ns
- ii. DFF propagation delay = 2 ns
- iii. XOR gate delay = 2 ns
- iv. MUX gate delay = 3 ns




4. Registers

a. Parallel register

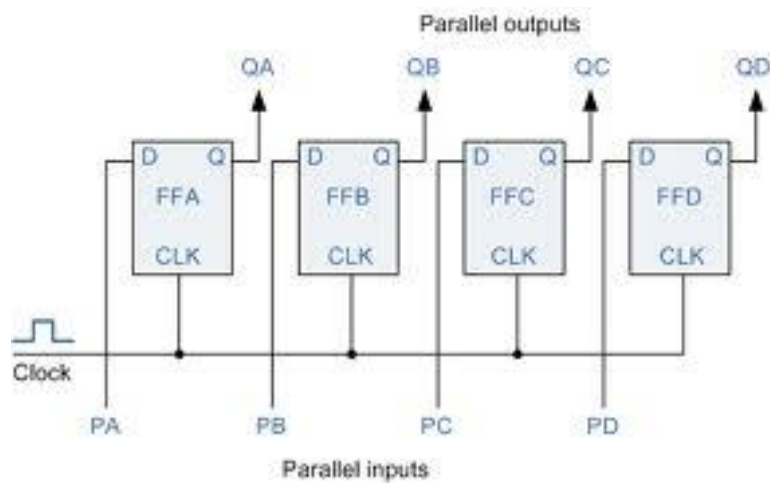

b. Shift register

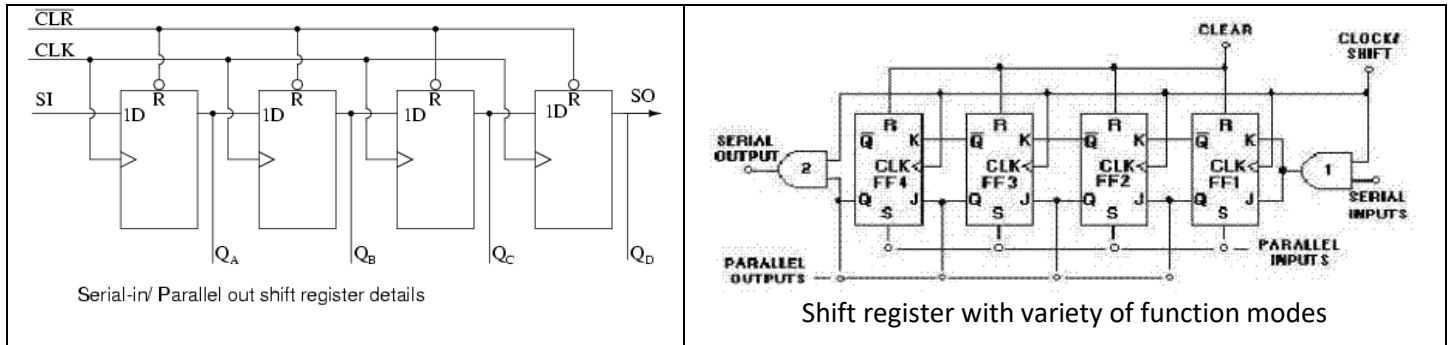

5. Counter

- a. Eventually “saturates”
- b. Ripple (asynchronous) counters
- c. Synchronous counter

i. How example below counts

ii. Below: synchronous implementation using T flip flops

