

1. More on Karnaugh maps
 - a. Further example with don't cares and wrapping
 - i. $f_3 = m_0 + D_2 + D_5 + D_7 + m_8 + m_{10}$


| | | <i>AB</i> | | | |
|-----------|----|-----------|----|----|----|
| | | 00 | 01 | 11 | 10 |
| <i>CD</i> | 00 | | | | |
| | 01 | | | | |
| | 11 | | | | |
| | 10 | | | | |

- b. Whether or not don't cares are included depends on your desired use case

2. Timing
 - a. Worst case path

- b. Timing diagram

 - c. Example
 - i. Implementation of XOR using only AND, OR, NOT on next page
 1. $A \oplus B = A * \sim B + \sim A * B$
 - ii. Assume that we have the following gate delays
 1. NOT = 3 ns
 2. AND = 5 ns
 3. OR = 4 ns
 - iii. What is the clock time of the circuit, if inputs become valid at time 0 ns?



| | | | | |
|--|--|--|--|--|
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |
| | | | | |


3. Combinational circuit building blocks

4. Multiplexors


a. Implementation

b. Example


i. 2 to 1 MUX

 

ii. 4 to 1 MUX

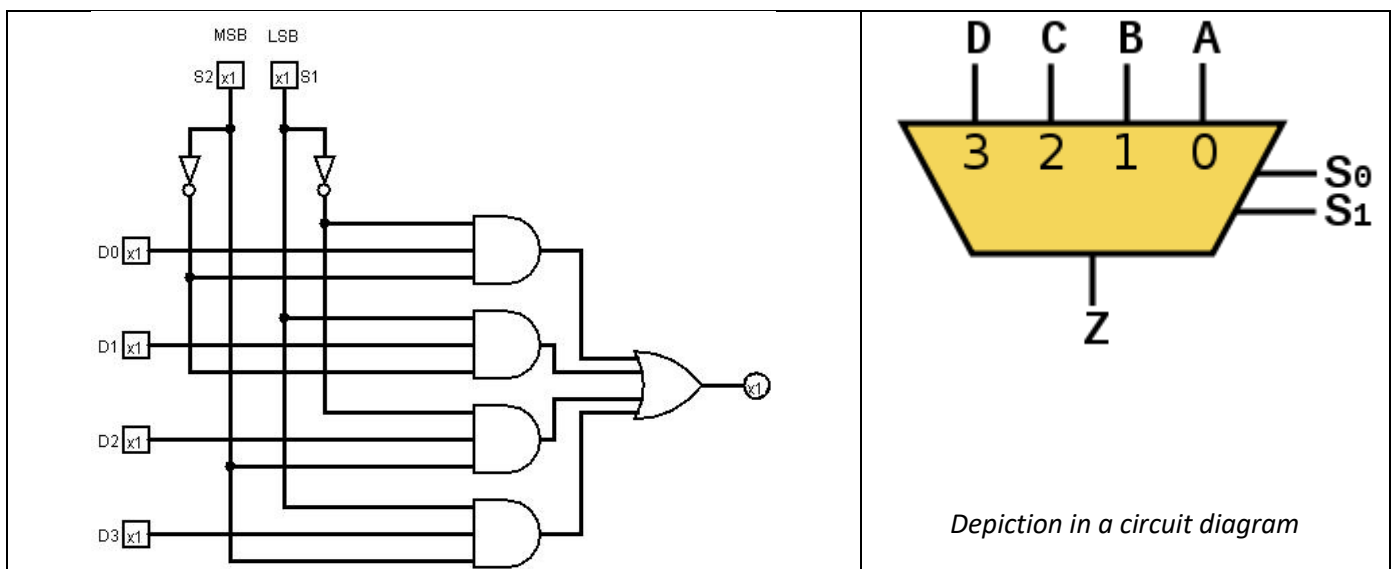

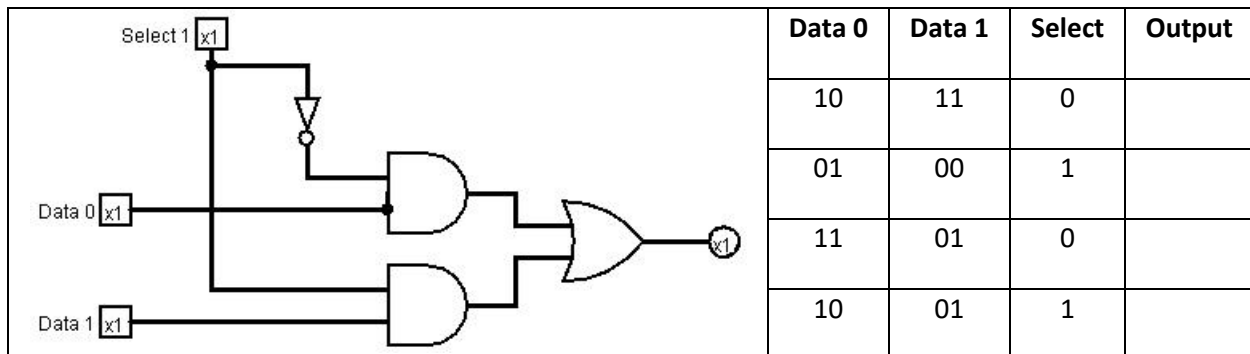- c. Truth table for simple 2-bit 2 to 1 MUX
i. Idealized picture below



- d. Can use MUXes to implement functions

