 


1. More logical equivalence examples

Laws of Logical Equivalence		
Name	OR version	AND version
<i>Commutative</i>	$A + B = B + A$	$A * B = B * A$
<i>Associative</i>	$(A + B) + C = A + (B + C)$	$(A * B) * C = A * (B * C)$
<i>Distributive</i>	$A + (B * C) = (A + B) * (A + C)$	$A * (B + C) = (A * B) + (A * C)$
<i>Idempotent</i>	$A + A = A$	$A * A = A$
<i>Identity</i>	$A + 0 = A$	$A * 1 = A$
	$A + 1 = 1$	$A * 0 = 0$
<i>Complement</i>	$A + \sim A = 1$	$A * \sim A = 0$
	$\sim 1 = 0$	$\sim 0 = 1$
<i>Double Negative</i>	$\sim(\sim A) = A$	
<i>De Morgan's</i>	$\sim(A + B) = \sim A * \sim B$	$\sim(A * B) = \sim A + \sim B$
<i>Absorption</i>	$A + (A * B) = A$	$A * (A + B) = A$

a. Prove the OR version of the Absorption Law,  $A + A * B = A$ .

b. Simplify the following digital logic circuit using propositional algebra.



$$f = ((A * \sim B) + (A * B)) * B \quad \text{Initial circuit logic}$$

2. More on gates

a. Functionally complete sets

i. AND, OR, NOT

ii. AND, NOT

iii. OR, NOT

iv. NAND -  $\uparrow$  is the NAND operator.

v. NOR -  $\downarrow$  is the NOR operator.

3. Truth tables

b. Minterms

c. Maxterms

d. Example: 3-variable Boolean function true when A is true, B is true, and C is false

- 4. Synthesizing using gates
  - e. Consider a Boolean function of three variables
    - i. True when either, but not both, of the first two variables is true

Index	A	B	C	$f(A, B, C)$	Minterm	Maxterm
0	0	0	0			
1	0	0	1			
2	0	1	0			
3	0	1	1			
4	1	0	0			
5	1	0	1			
6	1	1	0			
7	1	1	1			

- f. Sum-of-products
  - i. Can simplify using equivalence laws to reduce number of gates
- g. Product-of-sums
  - i. Can also simplify using laws of equivalence